

Shifting


Bit **Shifting** means to move bits left or right inside an operand.

There are two ways to shift the bits in an operand

1. **Logical shift:** fills the newly created bit position with zero



 2. **Arithmetic shift:** fills the newly created bit position is with a copy of the sign bit
(shift *arithmetic* right preserves the sign bit)



note: 'shift arithmetic left' works the same way as 'logical shift left', we can simply say Shift Left

Shifting

Arithmetic right shift: shift all bits to the right
preserves the sign bit
fills the MSB with a copy of the original sign bit

Right Shift = Division by powers of 2

$$a \gg n = \left\lfloor \frac{a}{2^n} \right\rfloor$$

```
user@host $ cat shift_s.py
num = 128
for i in range(10):
    print( num )
    num = num >> 1

user@host $ python shift_s.py
128
64
32
16
8
4
2
1
0
0
user@host $
```

Shift Left:



Shifting any operand left by n bits multiplies the operand by 2^n .

Example: shifting the integer 5 left by 1 bit yields the product of $5 * 2^1 = 10$:

Left Shift = multiplication by powers of 2

```
user@host $ cat shift.py
num = 5
print( num )
print( num << 1 )
print( num << 2 )
print( num << 3 )
```

```
user@host $ python shift.py
5
10
20
40
user@host $
```

Truth Tables

Order of Precedence

Precedence	Name	Operator	C++
1	Parentheses	()	()
2	NOT	'	!
3	AND	×	&&
4	XOR	\oplus	N/A
5	OR	+	

p	p'
0	1
1	0

NOT

Can only ever be 2 inputs. [0,1]

Number of inputs = x
Number of outputs = y

$$y = 2^n$$

p	q	p × q
0	0	0
0	1	0
1	0	0
1	1	1

AND

Number of inputs = 2
Number of outputs = 4

$$4 = 2^2$$

p	q	r	$p \times q \times r$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

AND

Number of inputs = 3

Number of outputs = 8

$$8 = 2^3$$

p	q	p + q
0	0	0
0	1	1
1	0	1
1	1	1

OR

Number of inputs = 2
Number of outputs = 4

$$4 = 2^2$$

p	q	r	p + q + r
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

OR

Number of inputs = 3

Number of outputs = 8

$$8 = 2^3$$

p	q	$p \oplus q$
0	0	0
0	1	1
1	0	1
1	1	0

XOR

Number of inputs = 2
Number of outputs = 4

$$4 = 2^2$$

p	q	r	$p \oplus q \oplus r$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

XOR

Number of inputs = 3

Number of outputs = 8

$$8 = 2^3$$

p	q	r	$p \times q + r$
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Try for yourself #1

Number of inputs = ?

Number of outputs = ?

? = $2^?$

p	q	r	$p \times (q + r)$
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Try for yourself #2

Number of inputs = ?

Number of outputs = ?


? = $2^?$

Building blocks: transistors & logic gates

Building blocks



Integrated Circuit
(IC)

 

logic gates




transistors

transistors





pushbutton - type of switch

 

instead of a finger to push the button
control input that turns the switch on or off

 A **digital circuit** has voltages that are treated as either *high* or *low*, high is labeled 1, low 0.



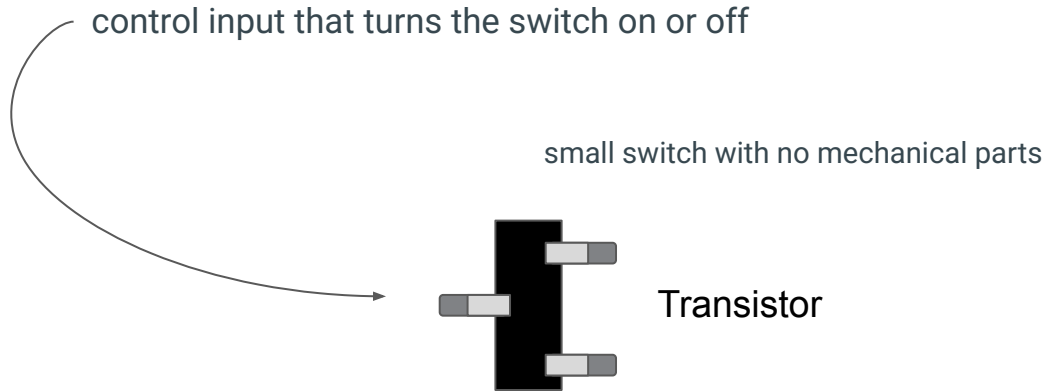

CMOS (Complementary Metal-Oxide-Semiconductor) technology uses pMOS and nMOS transistors to implement: microprocessors, microcontrollers, BIOS chips, and other digital circuits. CMOS technology is also used for image sensors.

Definition

nMOS conducts when control input is **1**

pMOS conducts when control input is **0**.

nMOS and pMOS transistors

CMOS


Gates:

NOT, NAND, AND, NOR, OR, XOR, XNOR




NOT Gate (inverter)

pMOS
does NOT conduct

 


nMOS
conducts

 

Inverter

NOT gate

pMOS
conducts

 


nMOS
does NOT conduct

Inverter

NOT gate

in	out
0	1
1	0

 

Inverter


NOT gate

NAND Gate

in1	in2	out
0	0	1
0	1	1
1	0	1
1	1	0



pMOS
conducts

 

nMOS
does NOT conduct




in1	in2	out
0	0	1
0	1	1
1	0	1
1	1	0



pMOS
conducts in1

pMOS does NOT
conduct in2

 

nMOS
conduct in2

nMOS does NOT
conduct in1




in1	in2	out
0	0	1
0	1	1
1	0	1
1	1	0



pMOS does NOT
conduct in1

pMOS
conduct in2

 

nMOS does NOT
conduct in2


nMOS
conducts in1



in1	in2	out
0	0	1
0	1	1
1	0	1
1	1	0



pMOS
does NOT conduct

 


nMOS
conducts



AND Gate

in1	in2	out
0	0	0
0	1	0
1	0	0
1	1	1

pMOS
conducts

 

nMOS does NOT
conduct


AND Gate

AND gate is built by inverting the output of a NAND gate
(due to physics: pMOS is a poor conductor of 0's, and nMOS a poor conductor of 1's)

in1	in2	out
0	0	0
0	1	0
1	0	0
1	1	1



pMOS
conducts for in1

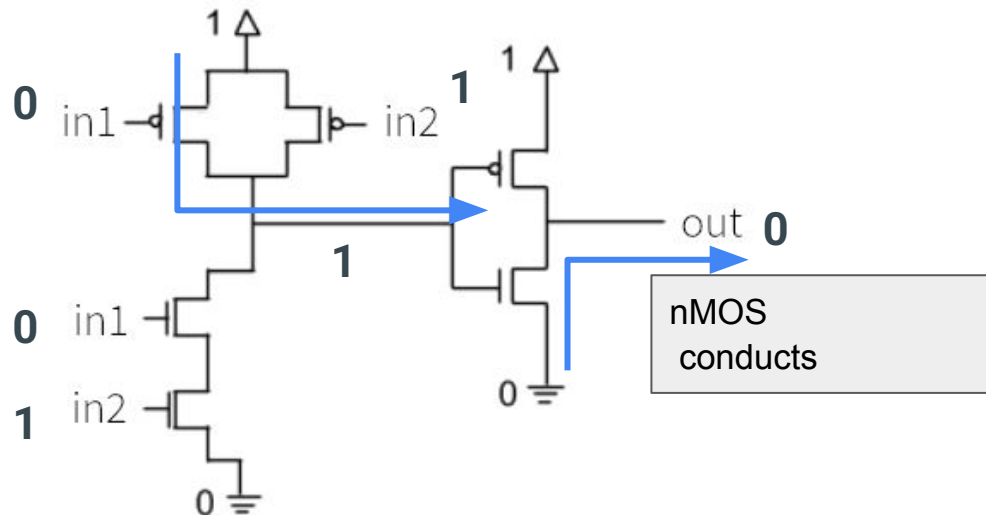

nMOS
conducts

nMOS does NOT
conduct for in1


AND Gate

AND gate is built by inverting the output of a NAND gate
(due to physics: pMOS is a poor conductor of 0's, and nMOS a poor conductor of 1's)

in1	in2	out
0	0	0
0	1	0
1	0	0
1	1	1



pMOS
conducts for in2

 

nMOS
conducts

nMOS does NOT
conduct for in2



AND Gate

AND gate is built by inverting the output of a NAND gate
(due to physics: pMOS is a poor conductor of 0's, and nMOS a poor conductor of 1's)

in1	in2	out
0	0	0
0	1	0
1	0	0
1	1	1



pMOS
does NOT conduct

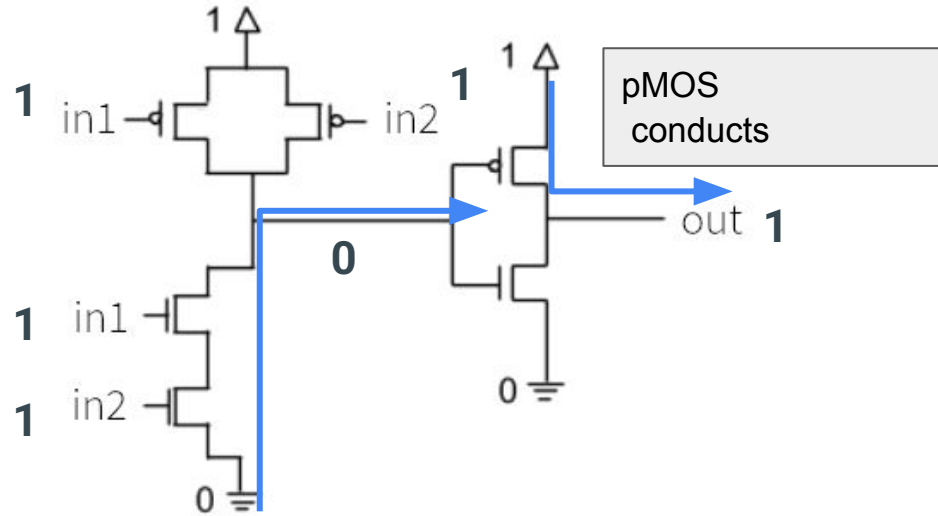 

nMOS
conducts

AND Gate


AND gate is built by inverting the output of a NAND gate
(due to physics: pMOS is a poor conductor of 0's, and nMOS a poor conductor of 1's)

NOR Gate

in1	in2	out
0	0	1
0	1	0
1	0	0
1	1	0



pMOS
conducts

 

nMOS does NOT
conduct




NOR Gate

in1	in2	out
0	0	1
0	1	0
1	0	0
1	1	0



pMOS does NOT
conduct for in2

 

nMOS
conducts for in2




NOR Gate


in1	in2	out
0	0	1
0	1	0
1	0	0
1	1	0



pMOS does NOT conduct for in1

 

nMOS conducts for in1

 


NOR Gate

in1	in2	out
0	0	1
0	1	0
1	0	0
1	1	0



pMOS
does NOT conduct

 

nMOS
conducts




NOR Gate

OR Gate

in1	in2	out
0	0	0
0	1	1
1	0	1
1	1	1



pMOS
conducts

 

nMOS
conducts

nMOS does NOT
conduct

OR Gate

OR gate is built by inverting the output of a NOR gate
 (due to physics: pMOS is a poor conductor of 0's, and nMOS a poor conductor of 1's)

pMOS does NOT
conduct for in2



OR Gate

OR gate is built by inverting the output of a NOR gate
(due to physics: pMOS is a poor conductor of 0's, and nMOS a poor conductor of 1's)


(due to physics: pMOS is a poor conductor of 0's, and nMOS a poor conductor of 1's)

(due to physics: pMOS is a poor conductor of 0's, and nMOS a poor conductor of 1's)

in1	in2	out
0	0	0
0	1	1
1	0	1
1	1	1



pMOS does NOT
conduct for in1

 


nMOS
conducts for in1

pMOS
conducts

OR Gate

OR gate is built by inverting the output of a NOR gate
(due to physics: pMOS is a poor conductor of 0's, and nMOS a poor conductor of 1's)

in1	in2	out
0	0	0
0	1	1
1	0	1
1	1	1

 


OR Gate

OR gate is built by inverting the output of a NOR gate
 (due to physics: pMOS is a poor conductor of 0's, and nMOS a poor conductor of 1's)

in1	in2	out
0	0	0
0	1	1
1	0	1
1	1	1



pMOS does NOT conduct

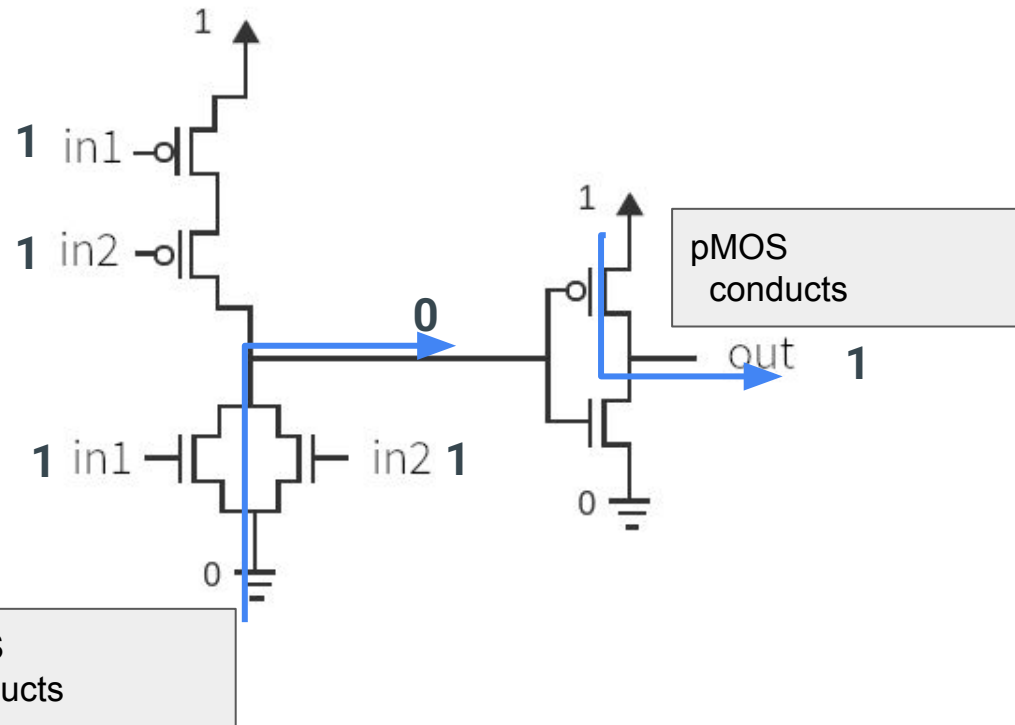

OR Gate


OR gate is built by inverting the output of a NOR gate
(due to physics: pMOS is a poor conductor of 0's, and nMOS a poor conductor of 1's)

XOR Gate (Exclusive-OR)

in1	in2	out
0	0	0
0	1	1
1	0	1
1	1	0



pMOS does NOT conduct in1, in2

 

nMOS conducts for in2, in1


XOR Gate

in1	in2	out
0	0	0
0	1	1
1	0	1
1	1	0



pMOS does NOT conduct in1, in2

pMOS conducts in1, in2

 

nMOS does NOT conduct in2, in1


XOR Gate

in1	in2	out
0	0	0
0	1	1
1	0	1
1	1	0



pMOS does NOT conduct in1, in2

 pMOS conducts $\overline{\text{in1}}$, in2




nMOS does NOT conduct in2, in1

XOR Gate

in1	in2	out
0	0	0
0	1	1
1	0	1
1	1	0



pMOS does NOT conduct in1, in2

 


nMOS conducts in2, in1

XOR Gate

XNOR Gate (Exclusive-NOR)

in1	in2	out
0	0	1
0	1	0
1	0	0
1	1	1

pMOS
conducts in1, in2

 


nMOS does NOT
conduct in2, in1

in1	in2	out
0	0	1
0	1	0
1	0	0
1	1	1



pMOS does NOT conduct in1, in2

 


nMOS conducts in2, in1

in1	in2	out
0	0	1
0	1	0
1	0	0
1	1	1



pMOS does NOT conduct in1, in2

 


nMOS conducts in2, in1

XNOR Gate

in1	in2	out
0	0	1
0	1	0
1	0	0
1	1	1

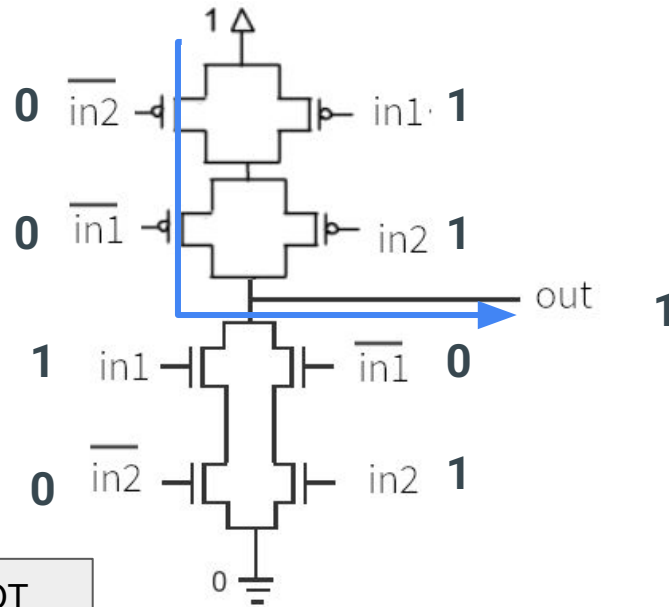pMOS
conducts $\overline{\text{in1}}$, $\overline{\text{in2}}$



nMOS does NOT
conduct $\overline{\text{in2}}$, $\overline{\text{in1}}$

XNOR Gate