


# Simplification

## Two-level combinational logic simplification


# Two-level combinational logic simplification
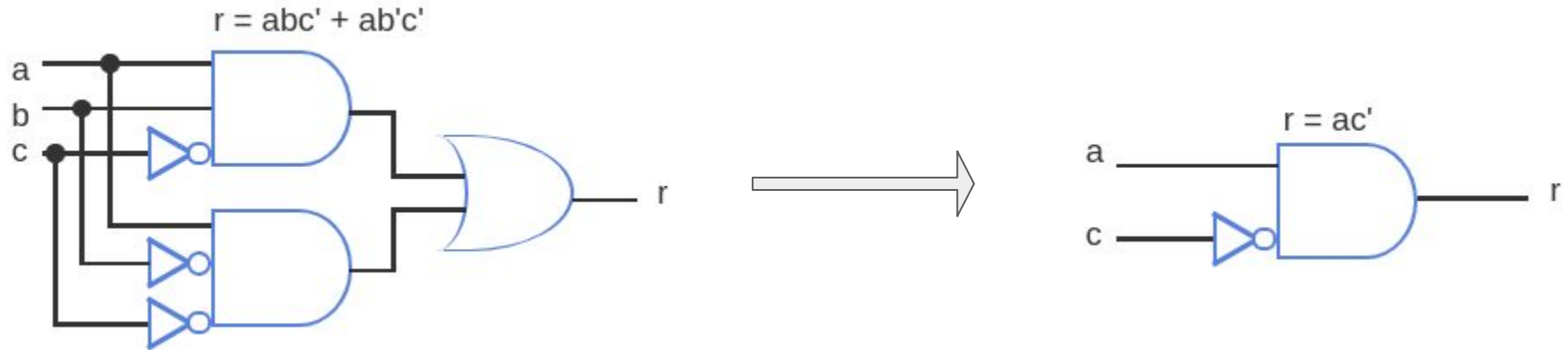
## Logic simplification

Logic simplification (also referred to as logic minimization) means to simplify a Boolean expression before converting to a circuit to yield a smaller circuit.


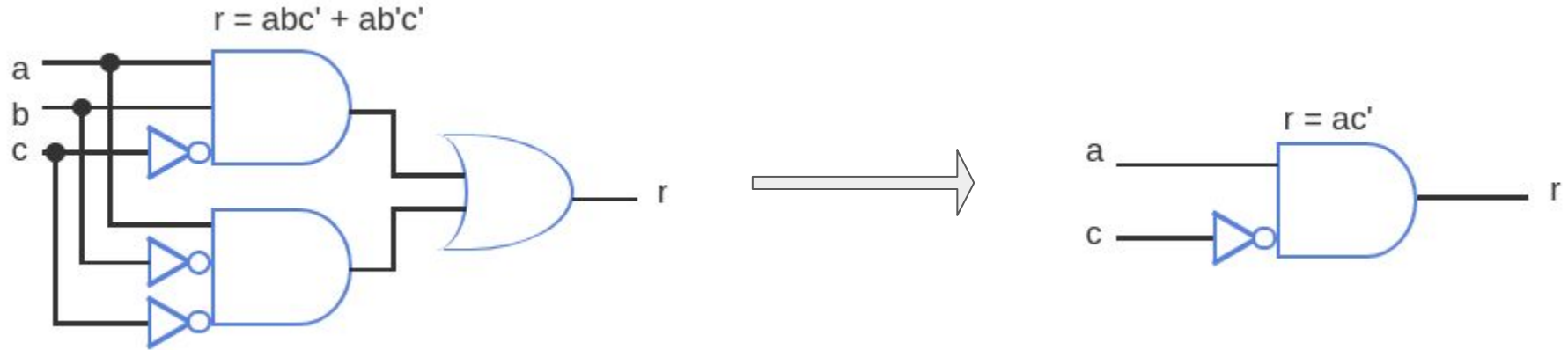
# Two-level combinational logic simplification



$$r = abc' + ab'c'$$

$$r = ac'(b + b')$$

$$r = ac'(1)$$

$$r = ac'$$

Distributive  
Complement  
Identity

# Two-level combinational logic simplification

Simplifying algebraically can be hard, a *designer may not see any opportunity* to simplify.

1) To help with this process, a designer converts to *sum-of-minterms* form.

2) designer must create  $i(j + j')$  opportunities by **replicating a term**.

Note: The need for such replication may not be obvious.

3) Then the designer must apply  $i(j + j')$  simplifications.

Again, the places where  $i(j + j')$  can be applied aren't obvious.

$$ab + a'$$

$$ab + a'(1) \quad \text{by Identity}$$

$$ab + a'(b + b') \quad \text{by Complement}$$

$$ab + a'b + a'b' \quad \text{by Distributive}$$

$$ab + a'b + a'b + a'b' \quad \text{by Idempotent}$$

$$(a + a')b + a'(b + b') \quad \text{by Distributive}$$

$$(1)b + a'(1) \quad \text{by Complement}$$

$$a' + b$$

Identity and Commutative

## K-map (Karnaugh map) simplification

help us to make  $i(j + j')$  simplification opportunities obvious

# K-map map simplification

A **K-map** is a graphical function representation that *eases the simplification process* for expressions involving a few variables, by adjacently placing minterms that differ in exactly one variable.

Let us consider a function of **two** variables a,b:  $y = a'b' + ab'$

Our K-map consists of four cells:

two rows (for  $a = 0$  and  $a = 1$ ).

two columns (for  $b = 0$  and  $b = 1$ )

	a	b	y
a'b'	0	0	1
a'b	0	1	0
ab'	1	0	1
ab	1	1	0

		b	
		0	1
a	0	1	0
	1	1	0

K-map is short for *Karnaugh map* ([Karnaugh](#) wiki)

# K-map map simplification

A **K-map** is a graphical function representation that *eases the simplification process* for expressions involving a few variables, by adjacently placing minterms that differ in exactly one variable.

Let us consider a function of **two** variables  $a, b$ :  $y = a'b' + ab'$

Our K-map consists of four cells:

two rows (for  $a = 0$  and  $a = 1$ ).

two columns (for  $b = 0$  and  $b = 1$ )

a \ b	0	1
0	$a'b'$	$a'b$
1	$ab'$	$ab$

a \ b	0	1
0	1	0
1	1	0

$b'$

$$y = b'$$

to simplify using K-map:


- 1) circle adjacent cells that have 1
- 2) write a product term with the *differing* variable omitted

Because adjacent minterm cells differ in exactly one literal, K-map's key benefit is to make  $i(j + j')$  simplification opportunities obvious



# K-map map simplification

Practice:  $y = a'b' + ab' + ab$

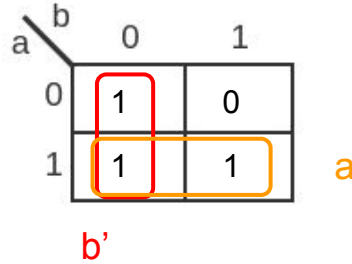

to simplify using K-map:

- 1) circle adjacent cells that have 1
- 2) write a product term with the differing variable omitted

a \ b	0	1
0	a'b'	a'b
1	ab'	ab

Therefore answer is  $y = a + b'$

# Expression simplification in programming

Computer programmers sometimes simplify expressions using **K-maps**.

For example: A program may make a decision based on an expression:

If ((isRed AND !isBlue) OR (!isRed AND isBlue) OR (isRed AND isBlue)) then take action X

The expression represents a function with two variables.  
Using a two-variable K-map, the programmer simplifies the expression, yielding:  
If (isRed OR isBlue) then take action X.

$a = \text{isRed}$   
 $b = \text{isBlue}$        $\rightarrow f(a,b) = ab' + a'b + ab$

Therefore  $y = a + b$

a \ b	0	1
0	a'b'	a'b
1	ab'	ab

a \ b	0	1	
a'b'	0	1	a'b
ab'	1	1	ab
	<b>b</b>		

**a**

# K-map map simplification

Let us consider a function of **three** variables  $a, b, c$ :  $f(a, b, c) = a'b'c + ab'c + abc' + abc$

Our K-map will consist of 8 cells:

two rows (for  $a = 0$  and  $a = 1$ ).

four columns (for  $bc = 00, bc=01, bc=11, bc=10$ )

		bc			
		00	01	11	10
a	0	$a'b'c'$	$a'b'c$	$a'bc$	$a'bc'$
	1	$ab'c'$	$ab'c$	$abc$	$abc'$

	a	b	c	f(a,b,c)
$a'b'c'$	0	0	0	0
$a'b'c$	0	0	1	1
$a'bc'$	0	1	0	0
$a'bc$	0	1	1	0
$ab'c'$	1	0	0	0
$ab'c$	1	0	1	1
$abc'$	1	1	0	1
$abc$	1	1	1	1

# K-map map simplification

Let us consider a function of *three* variables a,b,c:  $f(a,b,c) = a'b'c + ab'c + abc' + abc$

Our K-map will consist of 8 cells:

two rows (for  $a = 0$  and  $a = 1$ ).

four columns (for  $bc = 00, bc=01, bc=11, bc=01$ )

	a	b	c	f(a,b,c)
a'b'c'	0	0	0	0
a'b'c	0	0	1	1
a'bc'	0	1	0	0
a'bc	0	1	1	0
ab'c'	1	0	0	0
ab'c	1	0	1	1
abc'	1	1	0	1
abc	1	1	1	1

		bc			
a	bc	00	01	11	10
	0	0	1	0	0
1	0	0	1	1	1
1	1	0	1	1	1

# K-map map simplification

Let us consider a function of **three** variables  $a, b, c$ :  $f(a, b, c) = a'b'c + ab'c + abc' + abc$

To simplify using K-map: we circle adjacent cells containing **1** to form groups for simplification.  
But we will expand the rules that we used to group:

- size of the group must be a power of 2  $\rightarrow$  for function of 3 variable valid group sizes:  $2^0, 2^1, 2^2, 2^3$
- Groups should be as large as possible.  $\rightarrow$  start from highest power
- Every 1 must be in at least one group.  $\rightarrow$  circle a single 1 if it is not adjacent
- Overlapping allowed.
- Wrap around allowed.
- fewest number of groups

**Simplify:**  
write a product term with the differing variable omitted

		bc			
		00	01	11	10
a	0	0	1	0	0
	1	0	1	1	1

*Note: In the original image, the cell (a=0, bc=01) is circled in red, and the cells (a=1, bc=11) and (a=1, bc=10) are circled in orange.*

$b'c$

$ab$

Therefore  $f(a, b, c) = ab + b'c$

# K-map map simplification

Let us consider a function of **three** variables  $a, b, c$ :  $f(a, b, c) = a'b'c + ab'c + abc' + abc$

To simplify using K-map: we circle adjacent cells containing **1** to form groups for simplification.  
But we will expand the rules that we used to group:

- size of the group must be a power of 2 → for function of 3 variable valid group sizes:  $2^0, 2^1, 2^2, 2^3$
- Groups should be as large as possible. → start from highest power
- Every 1 must be in at least one group. → circle a single 1 if it is not adjacent
- Overlapping allowed.
- Wrap around allowed.
- fewest number of groups

**Simplify:**  
write a product  
term with the  
differing variable  
omitted

		bc			
		00	01	11	10
a	0	0	1	0	0
	1	0	1	1	1

		bc			
		00	01	11	10
a	0	$a'b'c'$	$a'b'c$	$a'bc$	$a'bc'$
	1	$ab'c'$	$ab'c$	$abc$	$abc'$

**Why is the above grouping not correct?**

# K-map map simplification

Let us consider a function of **three** variables  $a, b, c$ :  $f(a, b, c) = a'b'c + ab'c + abc' + abc$

To simplify using K-map: we circle adjacent cell containing **1** to form groups for simplification.  
But we will expand the rules that we used to group:

- size of the group must be a power of 2  $\rightarrow$  for function of 3 variable valid group sizes:  $2^0, 2^1, 2^2, 2^3$
- Groups should be as large as possible.  $\rightarrow$  start from highest power
- Every 1 must be in at least one group.  $\rightarrow$  circle a single 1 if it is not adjacent
- Overlapping allowed.
- Wrap around allowed.
- fewest number of groups

**Simplify:**  
write a product term with the differing variable omitted

		bc			
		00	01	11	10
a	0	0	1	0	0
	1	0	1	1	1

		bc			
		00	01	11	10
a	0	$a'b'c'$	$a'b'c$	$a'bc$	$a'bc'$
	1	$ab'c'$	$ab'c$	$abc$	$abc'$

**what is wrong with this grouping?**

# K-map map simplification

Let us consider a function of **three** variables  $a, b, c$ :  $f(a, b, c) = a'b'c + ab'c + abc' + abc$

To simplify using K-map: we circle adjacent cell containing **1** to form groups for simplification.  
But we will expand the rules that we used to group:

- size of the group must be a power of 2  $\rightarrow$  for function of 3 variable valid group sizes:  $2^0, 2^1, 2^2, 2^3$
- Groups should be as large as possible.  $\rightarrow$  start from highest power
- Every 1 must be in at least one group.  $\rightarrow$  circle a single 1 if it is not adjacent
- Overlapping allowed.
- Wrap around allowed.
- fewest number of groups

**Simplify:**  
write a product term with the differing variable omitted

		bc			
		00	01	11	10
a	0	0	1	0	0
	1	0	1	1	1

		bc			
		00	01	11	10
a	0	$a'b'c'$	$a'b'c$	$a'bc$	$a'bc'$
	1	$ab'c'$	$ab'c$	$abc$	$abc'$

how about now, why is this not correct?



# K-map map simplification

Let us consider a function of **three** variables  $a, b, c$ :  $f(a, b, c) = ab'c' + a'b'c'$

$$\text{Therefore } f(a, b, c) = b'c'$$

- size of the group must be a power of 2  $\rightarrow$  for function of 3 variable valid group sizes:  $2^0, 2^1, 2^2, 2^3$
- Groups should be as large as possible.  $\rightarrow$  start from highest power
- Every 1 must be in at least one group.  $\rightarrow$  circle a single 1 if it is not adjacent
- Overlapping allowed.
- Wrap around allowed.
- fewest number of groups

		bc			
		00	01	11	10
a	0	1	0	0	0
	1	1	0	0	0

$b'c'$

**Simplify:**  
write a product  
term with the  
differing variable  
omitted

# K-map map simplification

Let us consider a function of **three** variables  $a, b, c$ :  $f(a, b, c) = a'b'c' + a'bc'$

$$\text{Therefore } f(a, b, c) = a'c'$$

- size of the group must be a power of 2  $\rightarrow$  for function of 3 variable valid group sizes:  $2^0, 2^1, 2^2, 2^3$
- Groups should be as large as possible.  $\rightarrow$  start from highest power
- Every 1 must be in at least one group.  $\rightarrow$  circle a single 1 if it is not adjacent
- Overlapping allowed.
- Wrap around allowed.
- fewest number of groups

$a'c'$

		bc			
		00	01	11	10
a	0	1	0	0	1
	1	0	0	0	0

**Simplify:**  
write a product  
term with the  
differing variable  
omitted

# K-map map simplification

Let us consider a function of **three** variables  $a, b, c$ :  $f(a, b, c) = a'b'c' + ab'c' + a'bc' + abc'$

$$\text{Therefore } f(a, b, c) = c'$$

- size of the group must be a power of 2  $\rightarrow$  for function of 3 variable valid group sizes:  $2^0, 2^1, 2^2, 2^3$
- Groups should be as large as possible.  $\rightarrow$  start from highest power
- Every 1 must be in at least one group.  $\rightarrow$  circle a single 1 if it is not adjacent
- Overlapping allowed.
- Wrap around allowed.
- fewest number of groups

$c'$

		bc			
		00	01	11	10
a	0	1	0	0	1
	1	1	0	0	1

**Simplify:**  
write a product  
term with the  
differing  
variables  
omitted

# K-map map simplification

Let us consider a function of **three** variables  $a, b, c$ :  $f(a, b, c) = a'b'c + a'bc + ab'c + abc$

- size of the group must be a power of 2  $\rightarrow$  for function of 3 variable valid group sizes:  $2^0, 2^1, 2^2, 2^3$
- Groups should be as large as possible.  $\rightarrow$  start from highest power
- Every 1 must be in at least one group.  $\rightarrow$  circle a single 1 if it is not adjacent
- Overlapping allowed.
- Wrap around allowed.
- fewest number of groups

		bc			
		00	01	11	10
a	0	0	1	1	0
	1	0	1	1	0

**Simplify:**  
write a product  
term with the  
differing  
variables  
omitted

# K-map map simplification

Consider a function of **three** variables  $a, b, c$  given as truth table:

simplify using K-map

a	b	c	$f(a,b,c)$
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

a \ bc	bc			
	00	01	11	10
0	0	0	0	0
1	1	0	0	1

# K-map map simplification

Let us consider a function of four variables  $a, b, c, d$ :  $y = a'b'c'd' + a'b'cd' + ab'c'd' + ab'cd'$

- size of the group must be a power of 2  $\rightarrow$  for function of 4 variable valid group sizes:  $2^0, 2^1, 2^2, 2^3, 2^4$
- Groups should be as large as possible.  $\rightarrow$  start from highest power
- Every 1 must be in at least one group.  $\rightarrow$  circle a single 1 if it is not adjacent
- Overlapping allowed.
- Wrap around allowed.
- fewest number of groups

		cd			
		00	01	11	10
ab	00	1			1
	01				
	11				
	10	1			1

**Simplify:**  
write a product  
term with the  
differing  
variables  
omitted

# K-map map simplification

Let us consider a function of four variables a,b,c,d:  $y = a'bc'd + a'bcd + abc'd + abcd$

- size of the group must be a power of 2  $\rightarrow$  for function of 4 variable valid group sizes:  $2^0, 2^1, 2^2, 2^3, 2^4$
- Groups should be as large as possible.  $\rightarrow$  start from highest power
- Every 1 must be in at least one group.  $\rightarrow$  circle a single 1 if it is not adjacent
- Overlapping allowed.
- Wrap around allowed.
- fewest number of groups

		cd			
		00	01	11	10
ab	00				
	01		1	1	
	11		1	1	
	10				

**Simplify:**  
write a product  
term with the  
differing  
variables  
omitted

# K-map map simplification

Let's consider  $f(a,b,c,d) : y = a'b'c'd + a'b'cd + a'bc'd' + a'bcd' + abc'd' + abcd' + ab'c'd + ab'cd$

- size of the group must be a power of 2  $\rightarrow$  for function of 4 variable valid group sizes:  $2^0, 2^1, 2^2, 2^3, 2^4$
- Groups should be as large as possible.  $\rightarrow$  start from highest power
- Every 1 must be in at least one group.  $\rightarrow$  circle a single 1 if it is not adjacent
- Overlapping allowed.
- Wrap around allowed.
- fewest number of groups

		cd			
		00	01	11	10
ab	00		1	1	
	01	1			1
	11	1			1
	10		1	1	

**Simplify:**  
write a product  
term with the  
differing  
variables  
omitted