


# Homework Assignment 5 Answered

pMOS  conducts when the incoming voltage is low (0)

nMOS  conducts when the incoming voltage is high (1)


**Parallel – just one semiconductor needs to conduct**

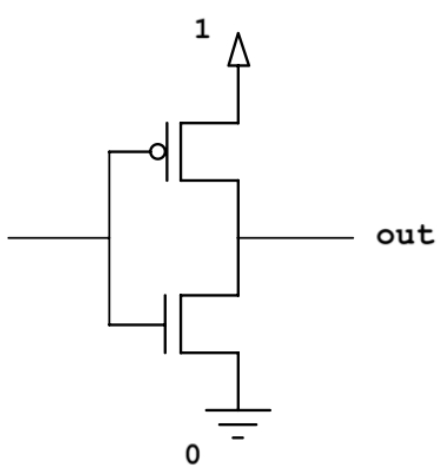**Series – all semiconductors need to conduct**



- If this CMOS inverter was given an input of 1, what would be the output? 0
- If this CMOS inverter was given an input of 0, what would be the output? 1
- What is the logical operation being performed? NOT
- Fill out its truth table.


in1	out
0	1
1	0

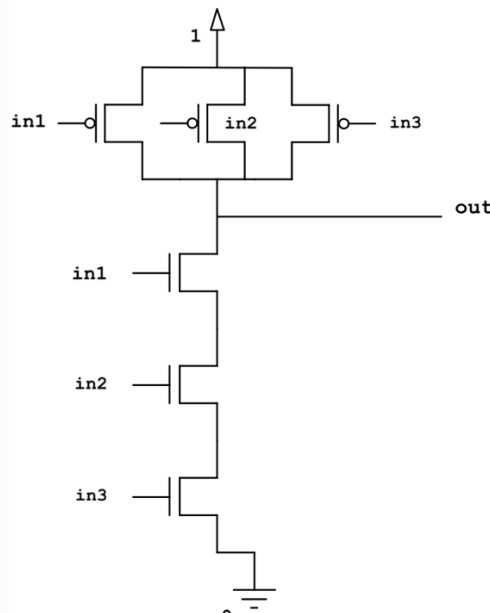

- Fill out the truth table for the gate on the left.

in1	in2	in3	out
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

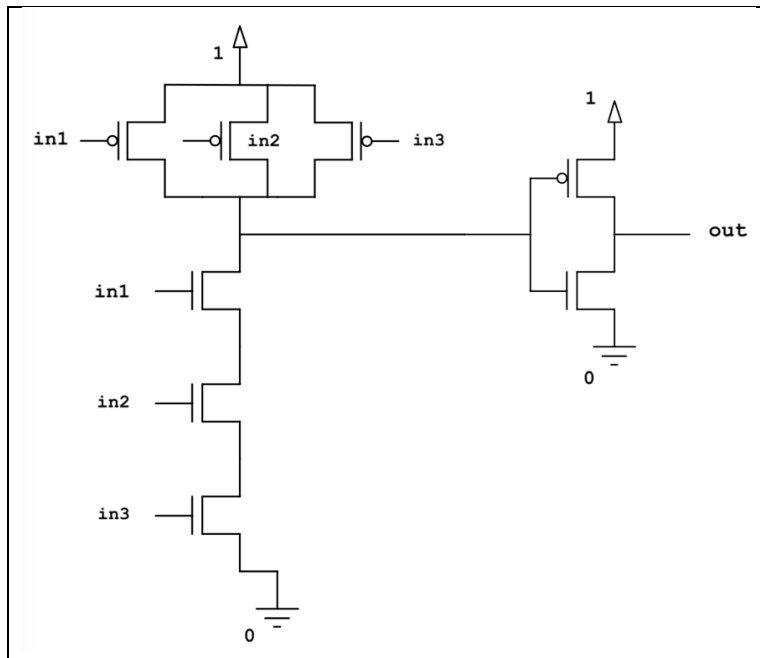
- What is the logical operation being performed? NAND



7. Fill out the truth table for the gate on the left.

in1	in2	in3	out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

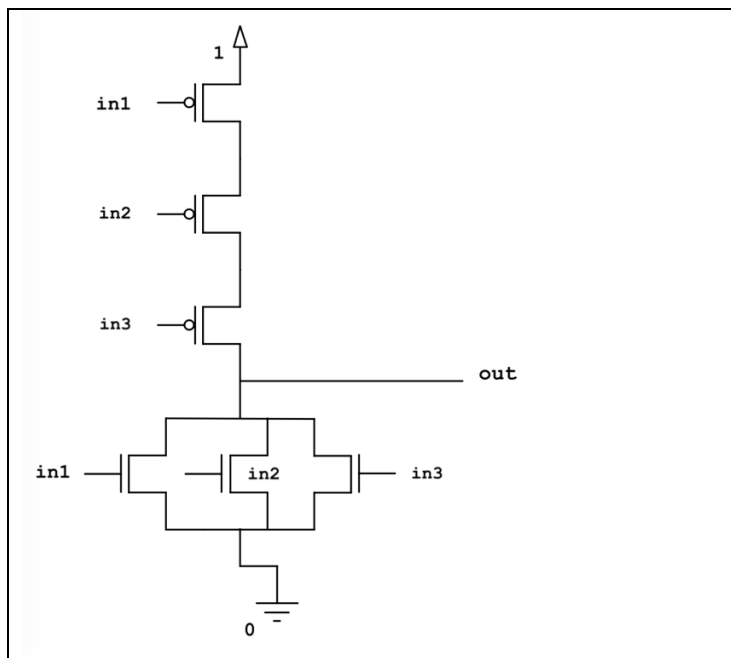8. What is the logical operation being performed? **AND**



9. Fill out the truth table for the gate on the left.

in1	in2	in3	out
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

10. What is the logical operation being performed? **NOR**

11. Fill out the truth table for the gate on the left.

in1	in2	in3	out
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

12. What is the logical operation being performed? **OR**

A	B	C	out
1	1	1	1
1	1	0	0
1	0	1	0
1	0	0	1
0	1	1	0
0	1	0	1
0	0	1	1
0	0	0	0

13. What is the final expression for the logic gate above?

$$\text{out} = ABC + AB'C' + A'BC' + A'B'C$$

14. What logical operation does the truth table appear to be equivalent to?

**XOR**